

DIGITAL STORAGE OSCILLOSCOPES

Part II: Oscilloscope probe and filter frequency response

Massimo Ortolano
2024

POLITECNICO DI TORINO

© 2011–2024 Massimo Ortolano

Dipartimento di Elettronica e Telecomunicazioni (DET)

Politecnico di Torino

Corso Duca degli Abruzzi, 24

10129 Torino

Italy



Email: massimo.ortolano@polito.it

This work is licensed under the Creative Commons Attribution-NonCommercial-ShareAlike 3.0 Unported License. To view a copy of this license, visit <http://creativecommons.org/licenses/by-nc-sa/3.0/> or send a letter to Creative Commons, 444 Castro Street, Suite 900, Mountain View, California, 94041, USA.



Team

Team no. B13

| Student | Last name | First name | Signature |
|---------|-----------|------------|---|
| 1 | Sakacı | Ali |  |
| 2 | Fuat | | |
| 2 | Unver | Muzaffer |  |
| 3 | Murathan | | |
| 4 | | | |

1 Assignment

In this lab you will practice with a digital storage oscilloscope (DSO) and its usage to measure the frequency response of filters.

Fill the PDF form and upload it on *Portale della didattica*, one upload for each team, by 29 April 2024.

2 Step response of an *RC* low-pass filter

2.1 Assembling the circuit

- 1 Assemble the circuit of figure 1 on the breadboard. Figure 2 shows a possible way of assembling the circuit.
- 2 Turn on the function generator Hantek HDG2032B and the oscilloscope.

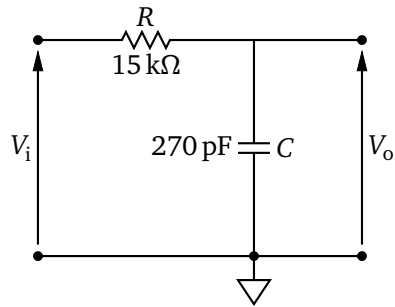


Figure 1: Circuit diagram of the RC filter.

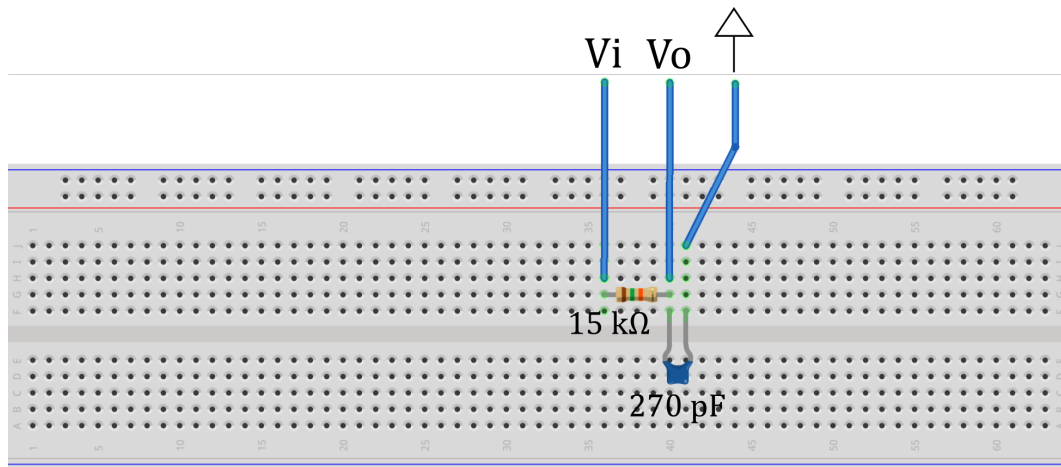


Figure 2: A possible way of assembling the RC filter of figure 1.

2.2 Rise-time and cut-off frequency (Coaxial cable)

- 1 Calculate the nominal cut-off frequency f_H for the circuit of figure 1. Calculate the nominal rise-time with the formula $t_r \approx 0.35/f_H$. Report the result in table 1 on the following page.
- 2 Using a BNC-to-BNC cable, a BNC T adapter and a coaxial cable with crocodile clips, connect the function generator output to the oscilloscope CH1 input and then to the circuit input V_i . **Warning:** The black clip is the ground.
- 3 Using a coaxial cable with crocodile clips, connect the circuit output V_o to the oscilloscope CH2 input.
- 4 Set the input coupling of both inputs to DC.
- 5 Set the function generator for a 1 kHz square wave. Measure the step-response rise time at the filter output and calculate the cut-off frequency from the formula $f_H \approx 0.35/t_r$. Report the results in table 1.
- 6 Compare the measured values with that obtained at point 1 above. Do they agree? How do you explain the results obtained? Comment below table 1.

Table 1: Filter's step-response with coaxial cable.

| | Theoretical | Measured |
|-------------------|-------------|------------|
| Rise time | | 11 μ s |
| Cut-off frequency | | 31818 Hz |

Comments:

Rise time can be seen on oscilloscope easily, all we need to do is apply the formula and find the cut-off frequency

2.3 Rise-time and cut-off frequency (Oscilloscope probe)

- 1 Disconnect the coaxial cable from the circuit output and the CH2 input and replace it with an attenuating oscilloscope probe (1 : 10 attenuation).
- 2 Compensate the probe (ask for a suitable screwdriver).
- 3 Measure the step-response rise time and calculate the cut-off frequency from the formula $f_H = 0.35/t_r$. Compare these values with the theoretical ones and those obtained in section 2.2. What can you conclude? Report the results in table 2 and comment below.

Table 2: Filter's step-response with the oscilloscope probe.

| | Theoretical | Measured |
|-------------------|-------------|--------------|
| Rise time | | 7,54 μ s |
| Cut-off frequency | | 46419 Hz |

Comments:

We can calculate by applying the same method but using the probe.

3 Frequency response of the RC low-pass filter

A generic linear time-invariant filter with voltage input and output (figure 3) is characterised by a transfer function

$$H(j2\pi f) = \frac{V_o}{V_i},$$

where V_i is the complex phasor associated with a sinusoidal input voltage at frequency f , and V_o is the phasor associated with the corresponding sinusoidal output voltage.

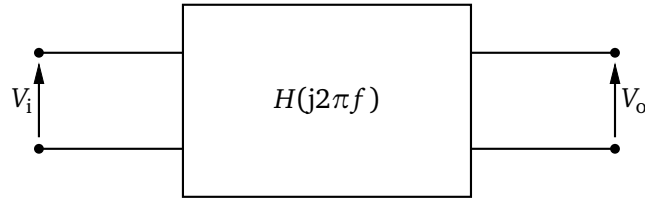


Figure 3:

$H(j2\pi f)$ is thus a complex number which changes with f . The Bode plots are graphical representations of the quantities $G(f) = 20 \log |H(j2\pi f)|$ and $\varphi(f) = \arg H(j2\pi f)$ as a function of the frequency (figure 4). $G(f)$ is the magnitude of the transfer function, expressed in decibel (dB), and $\varphi(f)$ is the phase. The frequency axis is logarithmic.

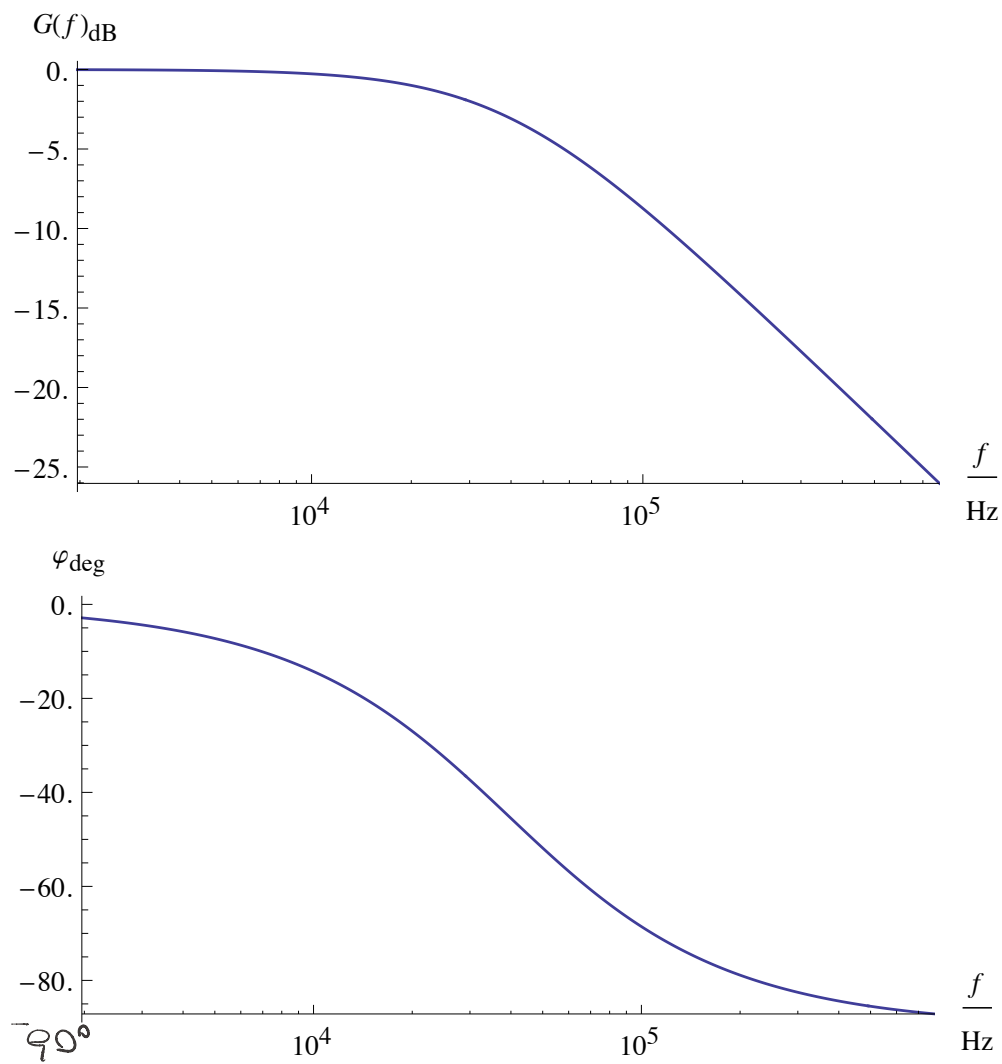


Figure 4: Example Bode plots.

- 1 Using the attenuating probe to connect the oscilloscope to the filter's output, measure $G(f)$ and $\varphi(f)$ for the filter assembled in §2.1 at the frequencies 1 kHz, 2 kHz, 5 kHz, 10 kHz, 20 kHz, 50 kHz, 100 kHz, 200 kHz and 500 kHz. Report the measurements in table 3.

Table 3: Measured transfer function of the RC filter.

| f/kHz | $G(f)$ | $\varphi(f)$ | $U(2\pi f)$ |
|----------------|--------|--------------|-------------|
| 1 | 0 | -1,8 | 1 |
| 2 | 0 | -3,6 | 1 |
| 5 | 0 | -9,7 | 1 |
| 10 | 0 | -15,13 | 1 |
| 20 | 0 | -21,43 | 1 |
| 50 | -3,09 | -47,9 | 0,7 |
| 100 | -7,13 | -59,4 | 0,44 |
| 200 | -12,4 | -79,92 | 0,24 |
| 500 | -18,41 | - | 0,12 |

